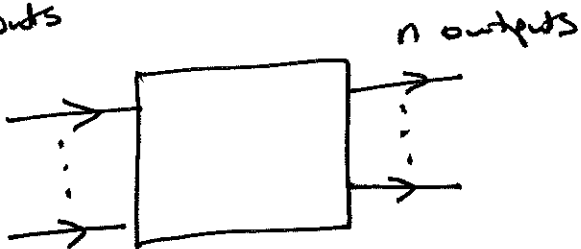


Lecture 24


Goal To show that every combinational circuit can be constructed from gates

m inputs




m inputs

1 output

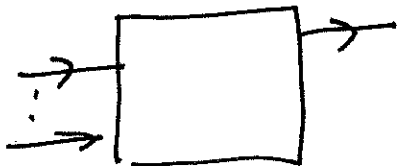

m inputs

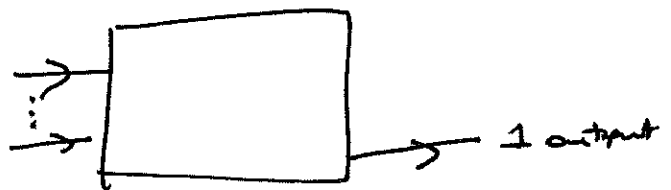





producing
n circuits ~~representing~~ each of n outputs

~~This will be our restriction on our attention to machines~~

~~with m inputs and n outputs.~~

We can combine two n circuits using fanout.

Example

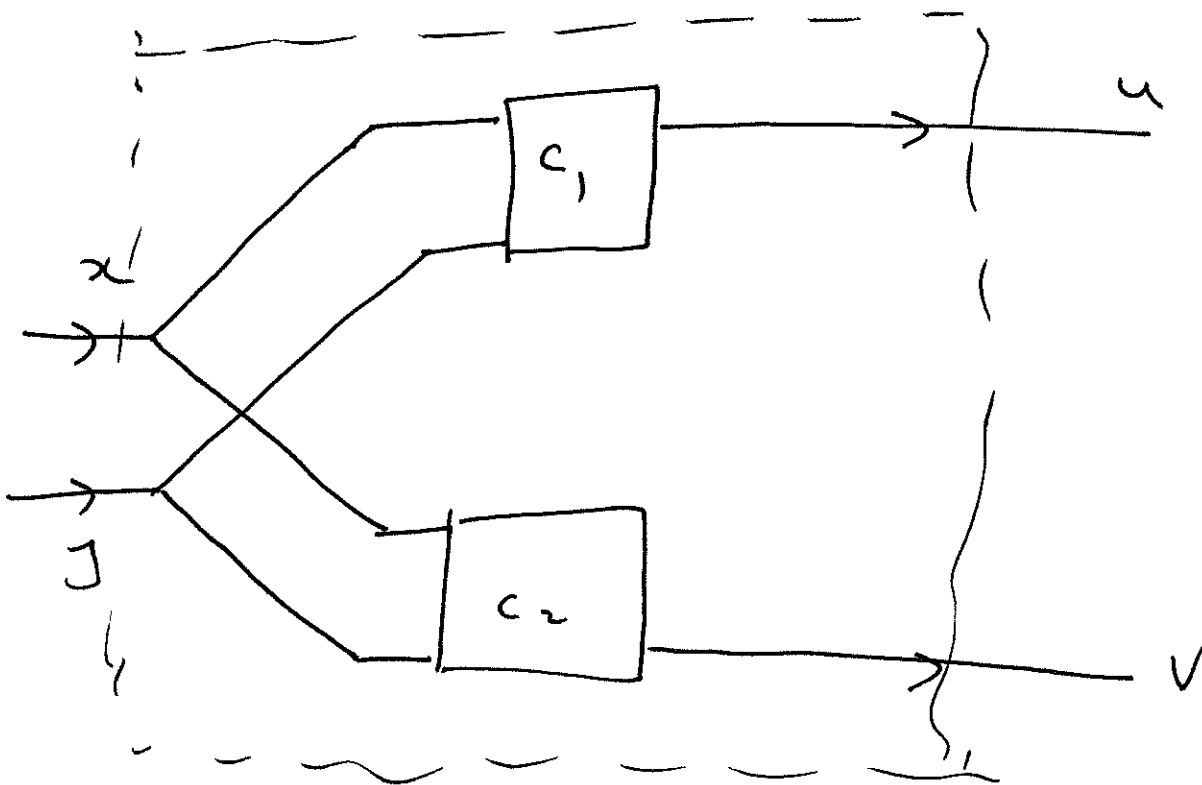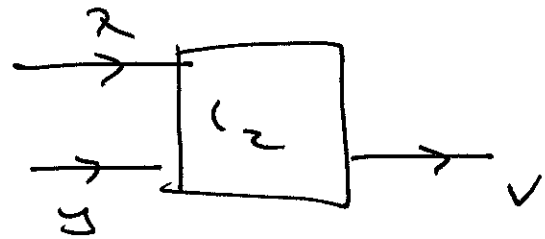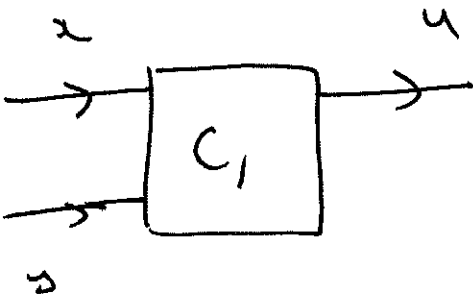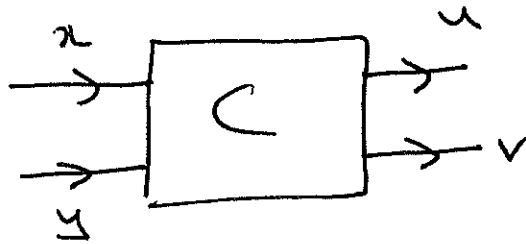

Thus we can restrict our attention to circuits with m -inputs and 1-output.

Example / Method Input/output table of
a combinational circuit.

input			output
x	y	z	w
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	0

Arrows point to rows 2, 4, and 6, which are labeled ①, ②, and ③ respectively.

Look at the places where the output is 1.

Write down what are called min terms

① $x y \bar{z}$

② $x \bar{y} z$

③ $\bar{x} y \bar{z}$

It follows that


$$u = xy\bar{z} + x\bar{y}\bar{z} + \bar{x}y\bar{z}$$

This is a Boolean expression that describes exactly the input/output behaviour.


We now convert this expression into a circuit — we should need to introduce brackets.

First, write down parse trees


$$(xy)\bar{z}$$

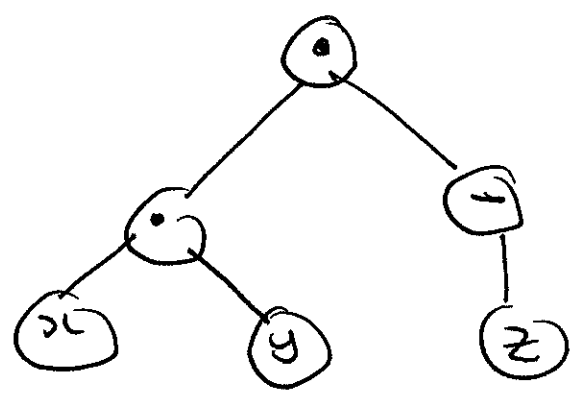


$(xy)\bar{z}$

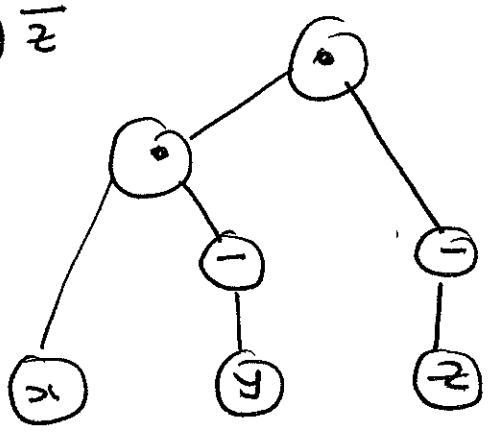


$(\bar{x}y)\bar{z}$

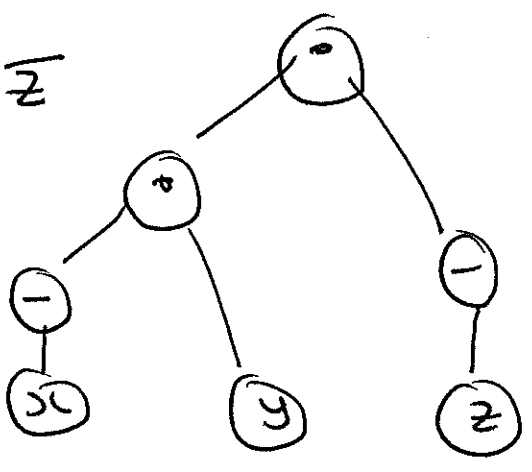


Next, rotate each tree 90° clockwise.

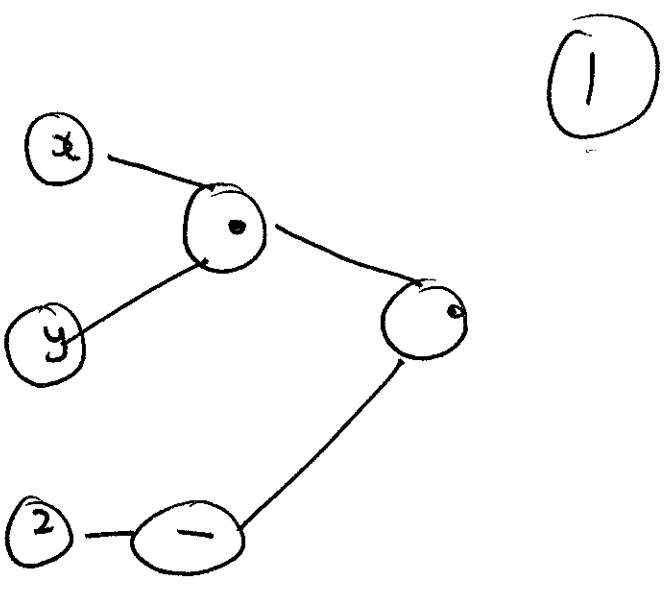

(2)

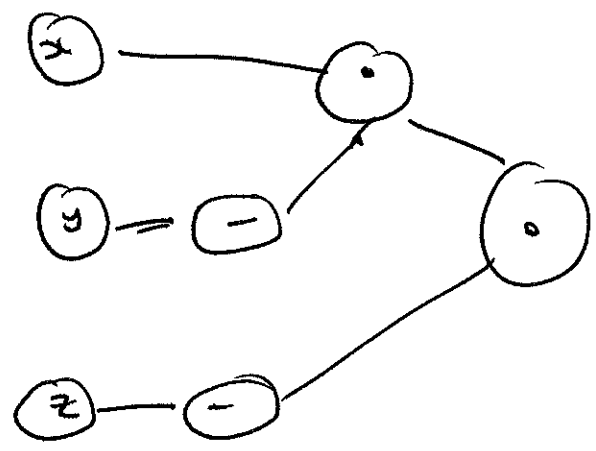


(3)

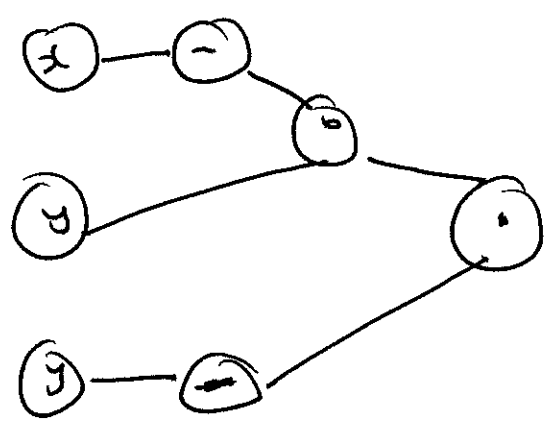


Now replace each Boolean operation by an appropriate gate.


1

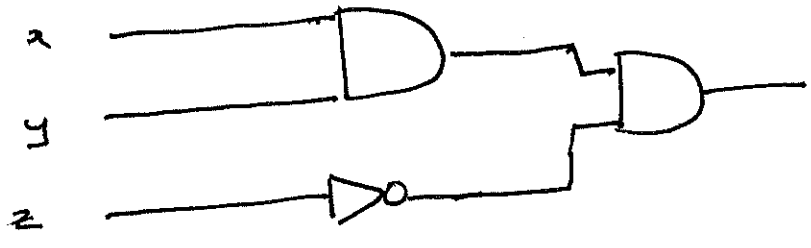

2

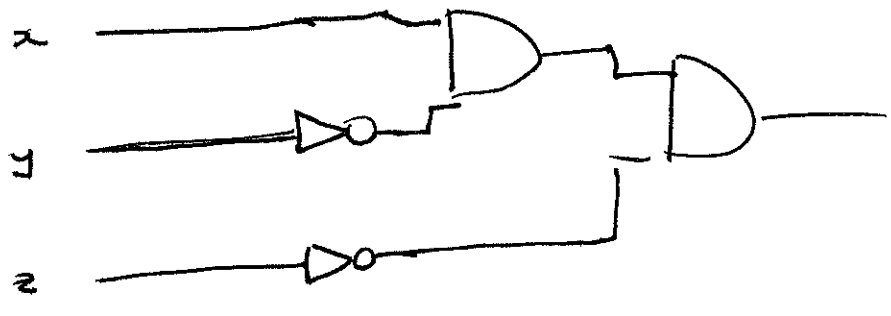


3

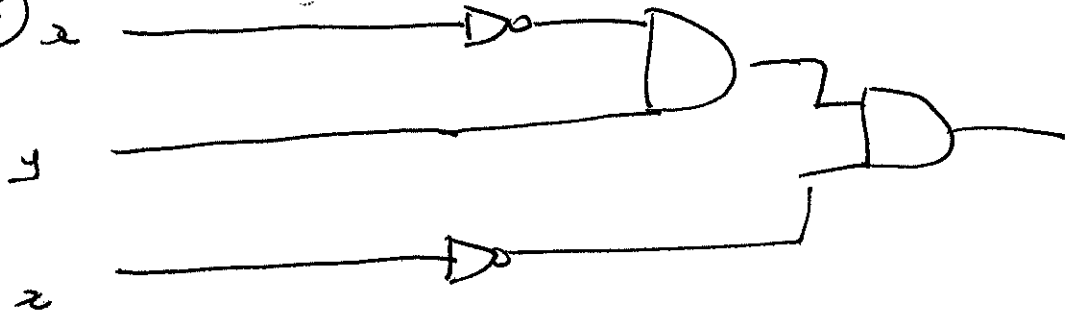

Now draw the three circuits using four 2 or-gates
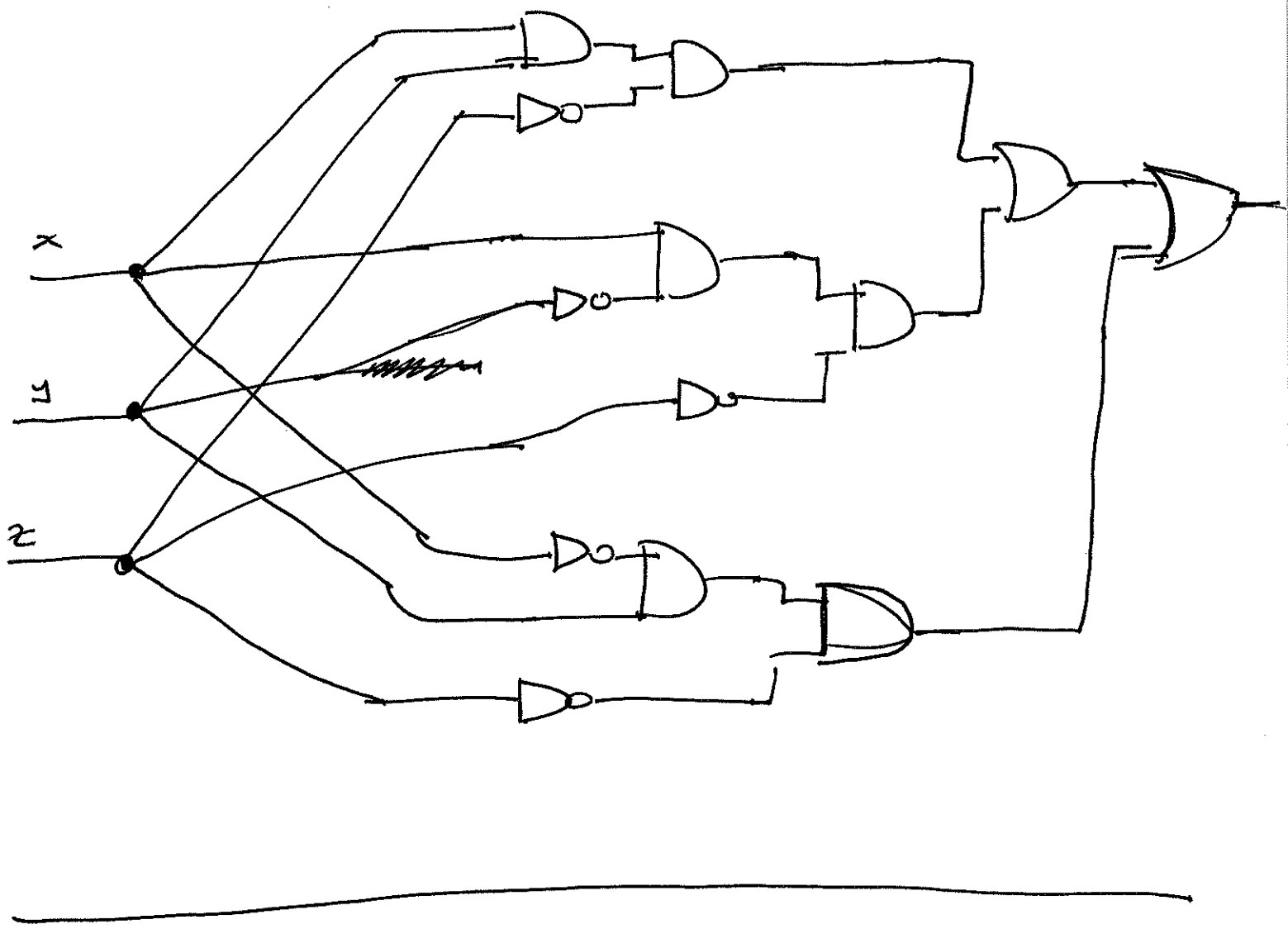
$$((xy)\bar{z} + (x\bar{y})z) + (\bar{x}y)z$$




Example


x	y	$x \oplus y$
1	1	0
1	0	1
0	1	1
0	0	0

$$x \oplus y = x\bar{y} + \bar{x}y$$


Parse tree

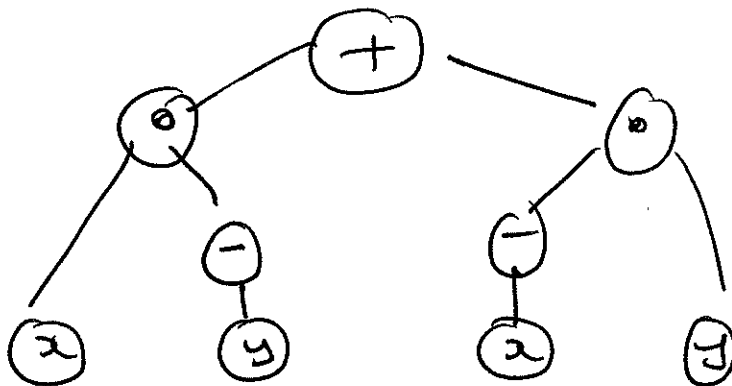

Circuit

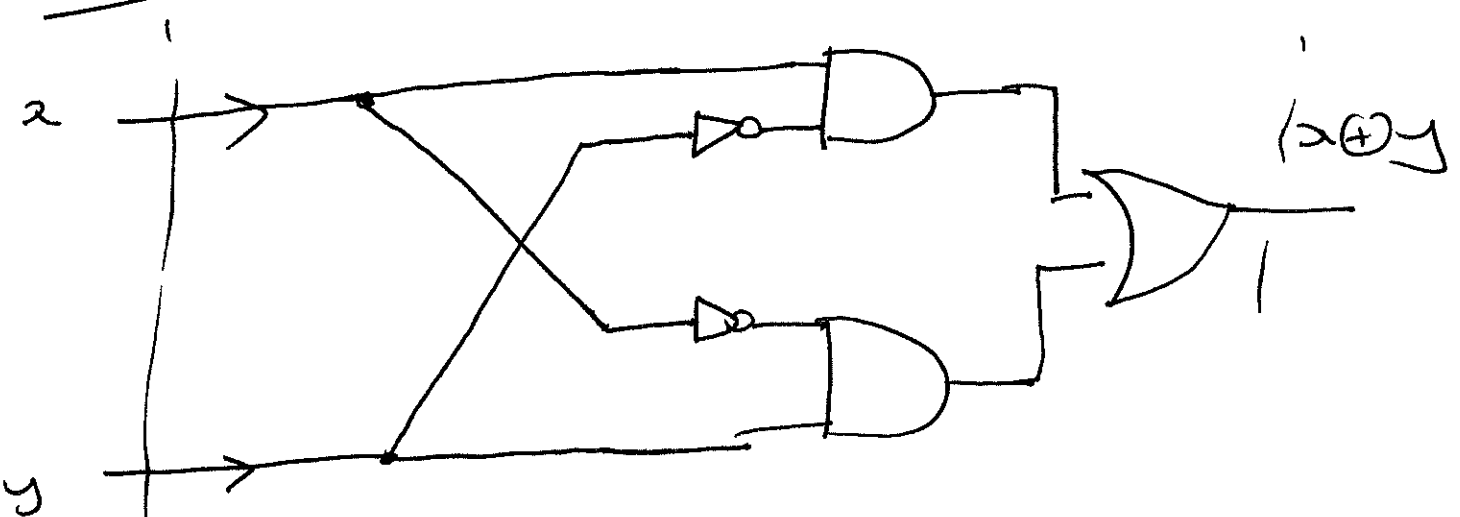


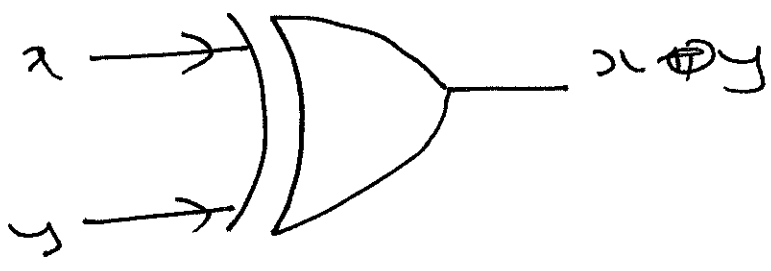This is exclusive-or and has its own symbol




Other gates

Nand-gates

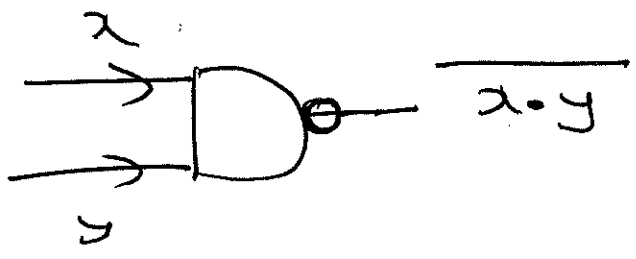

Nor gates

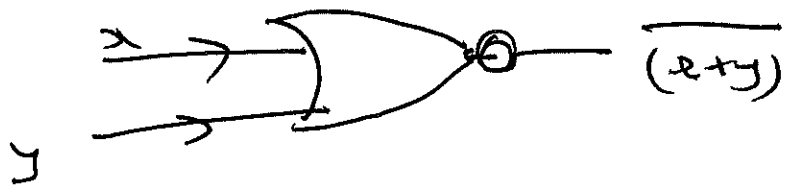


Using our work in PL

Theorem

- (1) Every combinational circuit can be constructed from and-gates, or-gates and not-gates
- (2) Every combinational circuit can be constructed from Nand-gates (or, Nor-gates).

Transistors

These are electronic switches

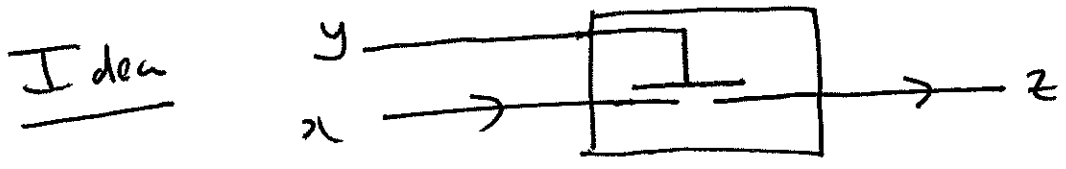

If $y = 0$ then $z = x$.

If $y = 1$ then $z = 0$.

Input/output table

x	y	$x \text{ } \square \text{ } y$
1	1	0
1	0	1
0	1	0
0	0	0

ad hoc symbol

$$x \text{ } \square \text{ } y = x \cdot \bar{y}$$

Theorem Every combinational circuit can be constructed from transistors.

Proof. Enough to show that transistors can be used to construct and-gates, or-gates, not-gates.

~~1 0 a = 1 \cdot \bar{a} = \bar{a}~~

- $1 \square a = 1 \cdot \bar{a} = \bar{a}$. not-gates.

- $a \square \bar{y} = a \cdot \overline{\bar{y}} = a \cdot y$ and gates

- ~~$(1 \square a) \square y$~~

$$1 \square [(1 \square a) \square y]$$

$$= \overline{1 \cdot ((1 \square a) \square y)}$$

$$= \overline{(1 \square a) \square y}$$

$$= \overline{\overline{(1 \bar{x}) \square y}}$$

$$= \overline{\overline{\bar{x} \square y}}$$

$$= \overline{\overline{\bar{x} \bar{y}}} = x + y \quad \text{or gates} \quad \square$$
